

DIGITAL SYSTEMS

PRACTICUM 4



By:

ALIF FAUZIA RAMA WAHYU


NIM: L200183177

INFORMATION TECHNOLOGY

FACULTY OF COMMUNICATION AND INFORMATICS

UNIVERSITY OF MUHAMMADIYAH SURAKARTA

Experiment 1.

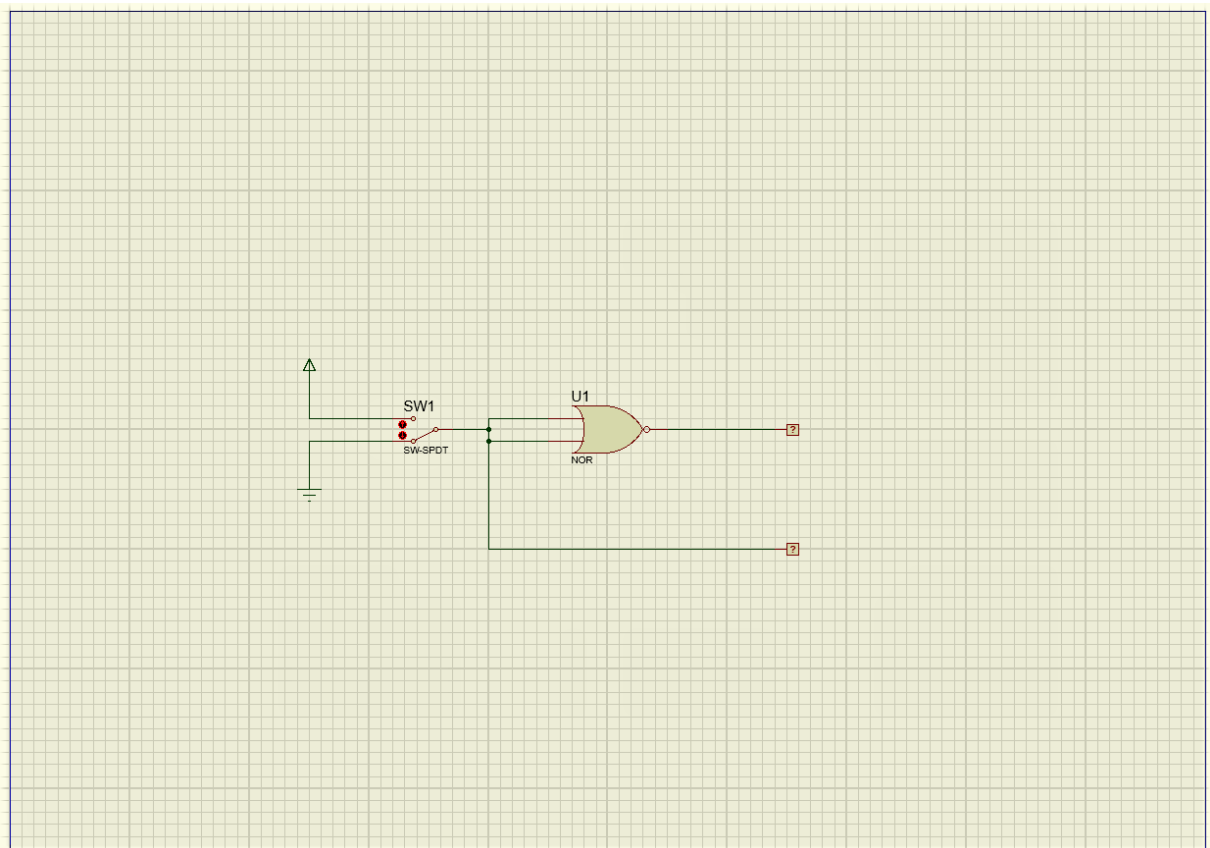

Picture 1.1. Gate 1 variation

1. Truth table

SW1	L2	L1
0	0	1
1	1	0

2. Time diagram

L1




L2



3. Conclusion

The NOR gate in picture 1.1 forms the logic of the NOT gate

Experiment 2.

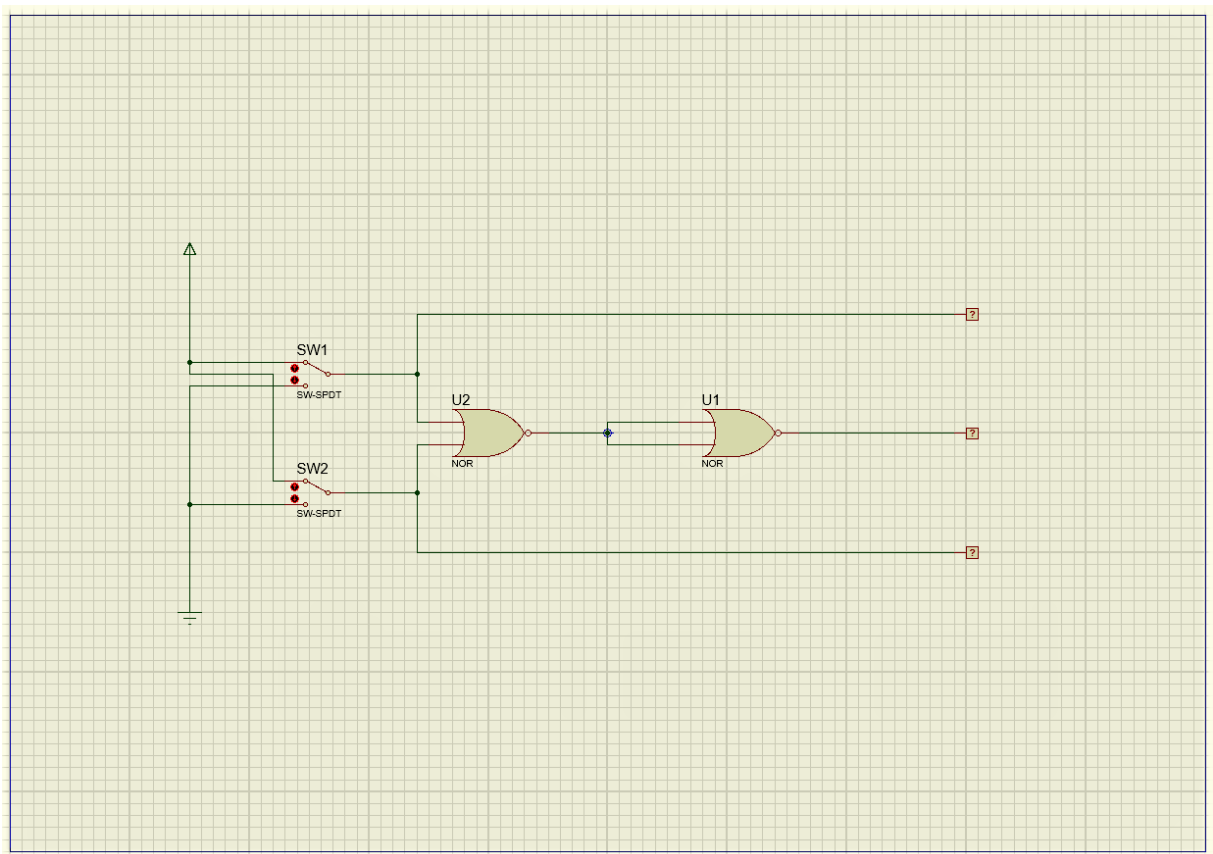


Picture 2.1. Gate 2 variation

1. Truth table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	1


2. Time diagram

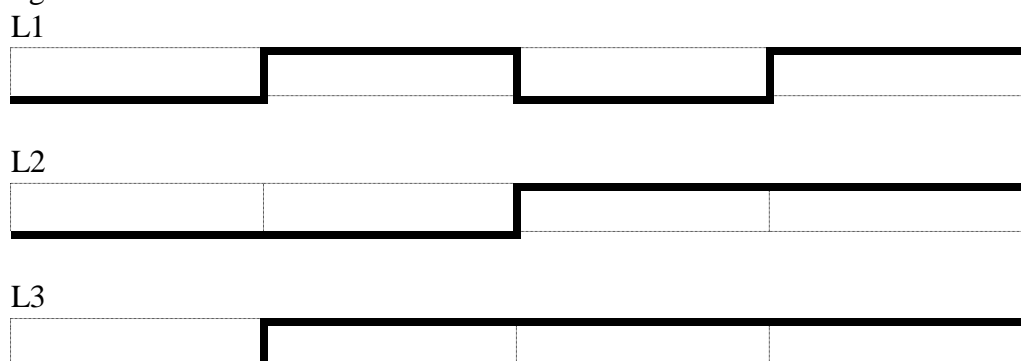

3. Conclusion

The NOR gate in picture 2.1 forms the logic of the OR gate

Experiment 3.

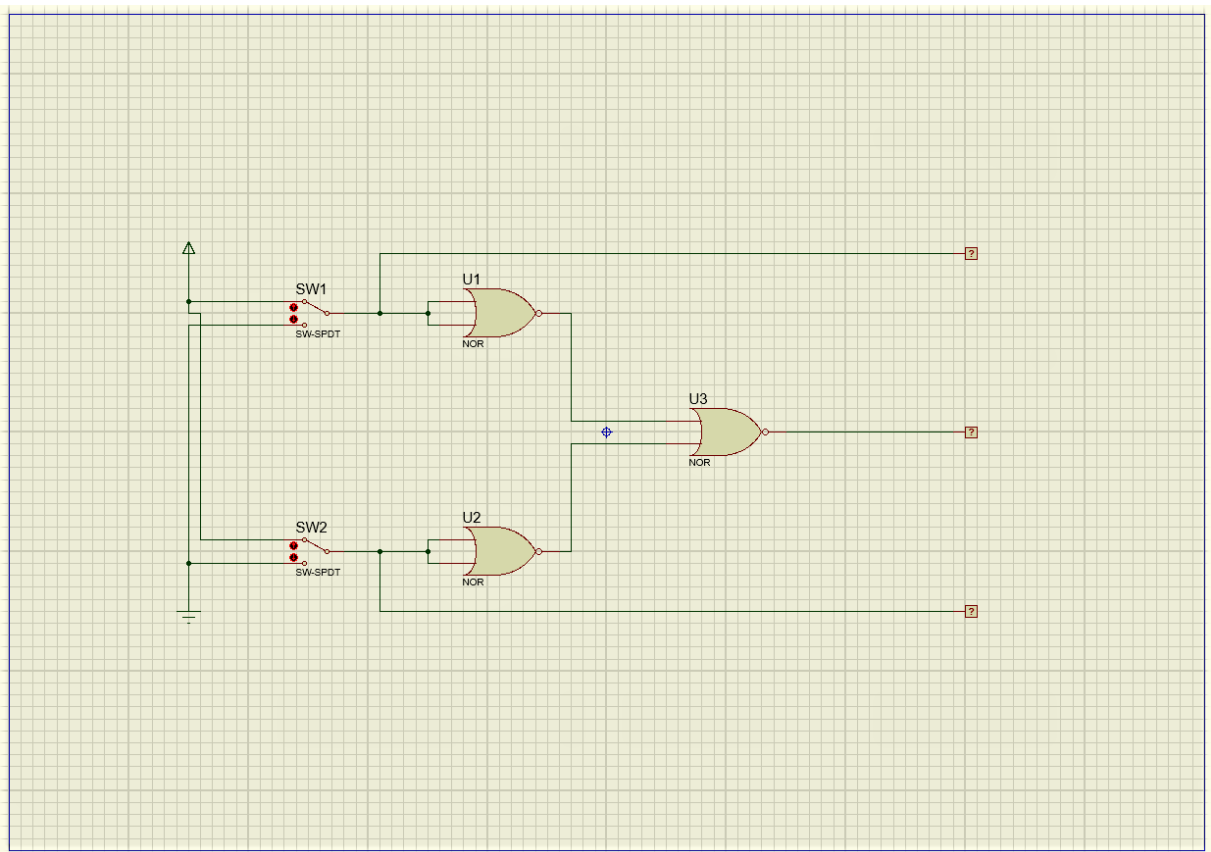

Picture 3.1. Gate 3 variation

1. Truth table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	0
0	1	0	1	0
1	1	1	1	1

2. Time diagram

L1



L2




L3



3. Conclusion

The NOR gate in picture 3.1 forms the logic of the AND gate

Experiment 4.

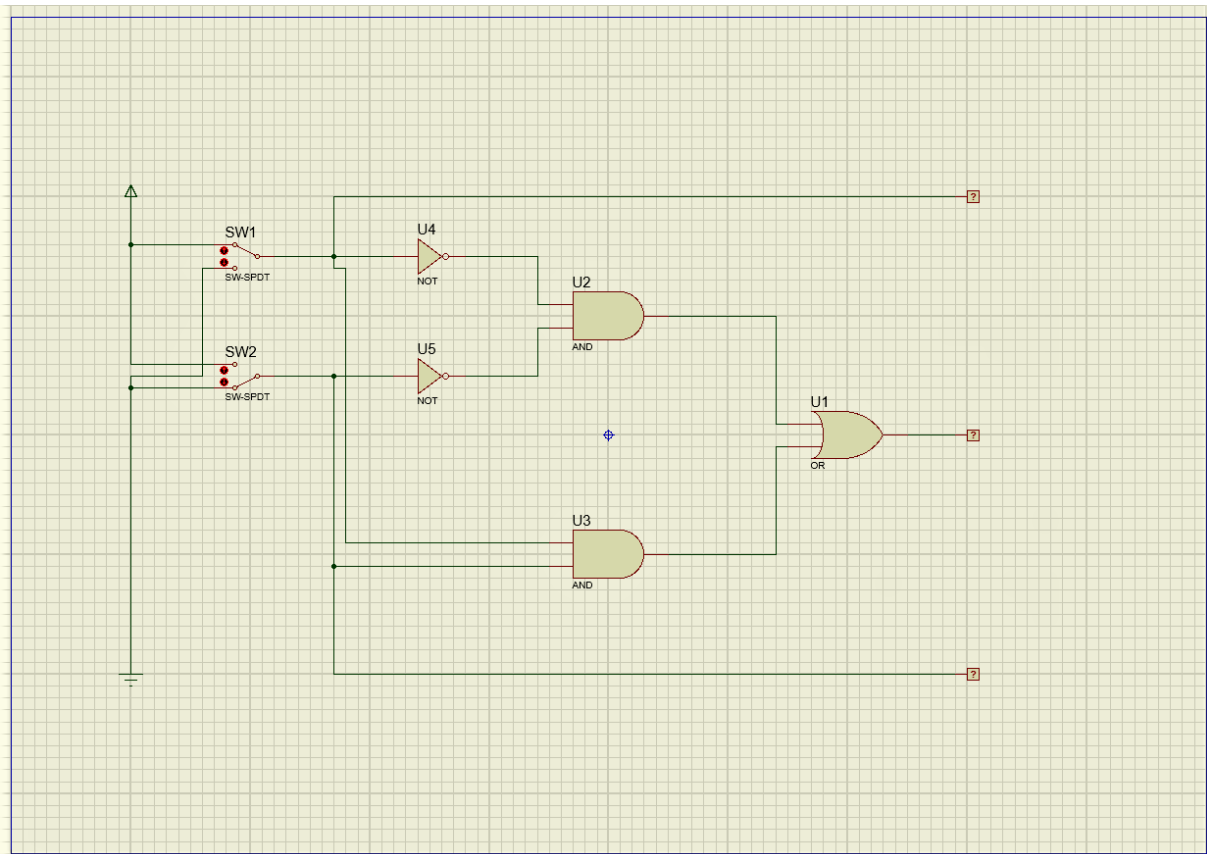

Picture 4.1. Gate 4 variation

1. Truth table

SW1	SW2	L1	L2	L3
0	0	0	0	1
1	0	1	0	0
0	1	0	1	0
1	1	1	1	1

2. Time Diagram

L1




L2



3. Conclusion

- The NOR gate in picture 4.1 forms the logic of the XNOR gate

Experiment 5.

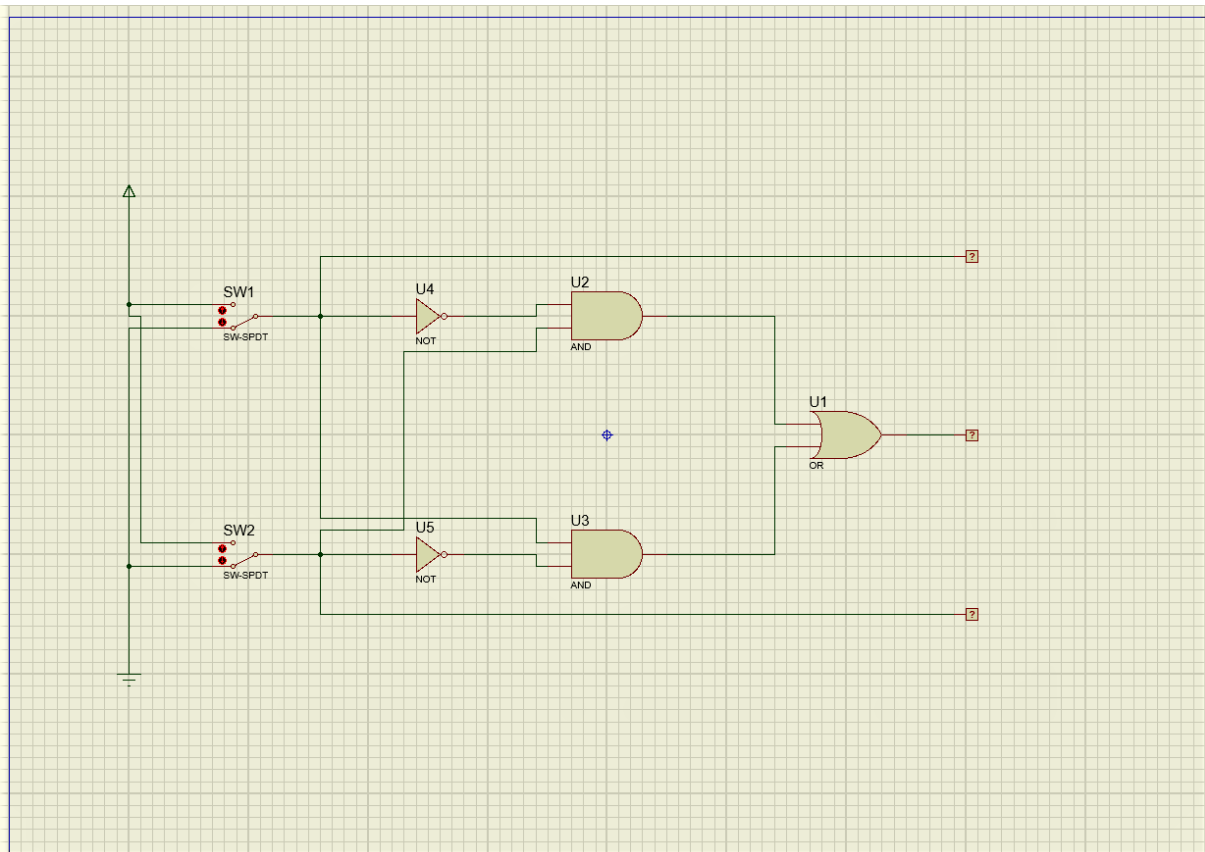

Picture 5.1. Gate 5 variation

1. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	0

2. Diagram Waktu

L1



L2




L3



3. Conclusion

The NOR gate in picture 4.1 forms the logic of the XOR gate

Additional Experiment 1.

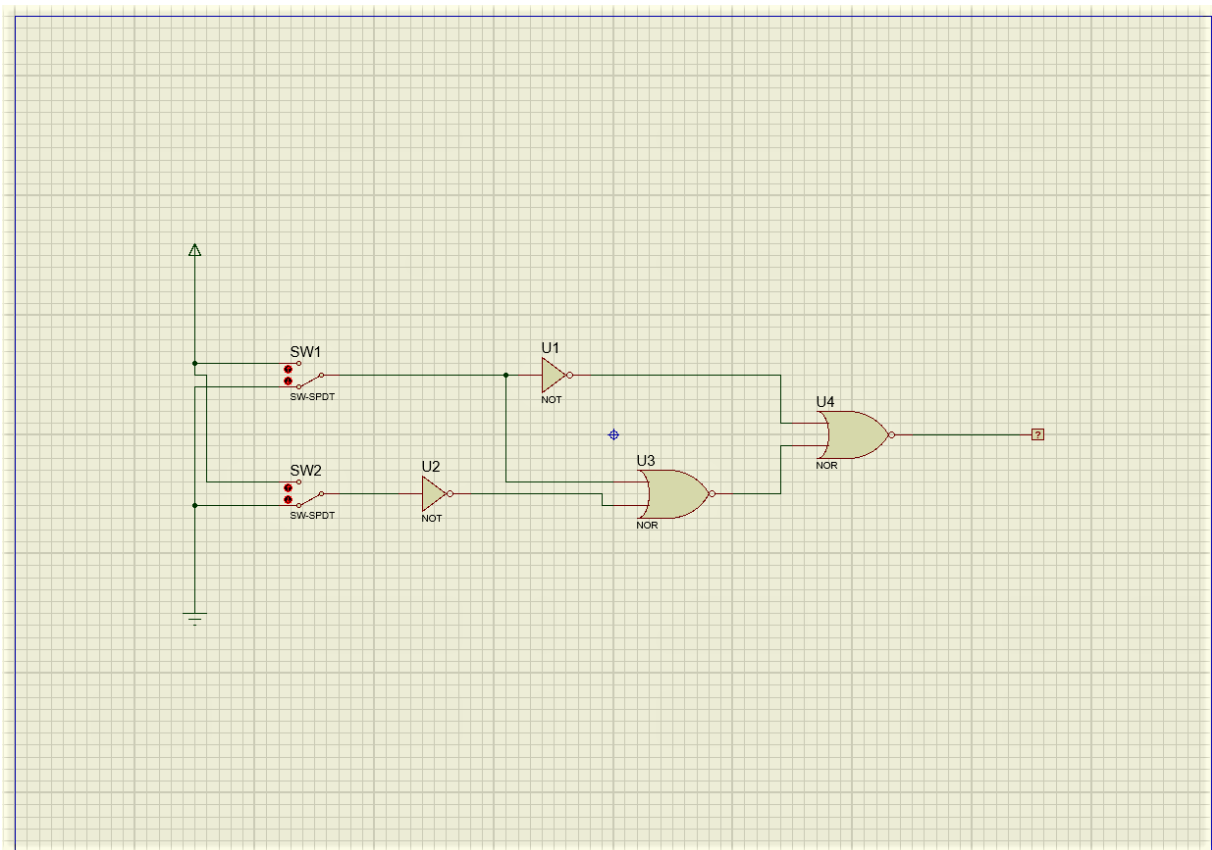

Picture 6.1. Set of gate

1. Truth Table

X	Y	F
0	0	0
0	1	0
1	0	1
1	1	1

2. Time Diagram


L1



3. Boolean Function

$$F = \neg(\neg X + \neg(X + \neg Y)) = X(X + \neg Y)$$

Additional Experiment 2.

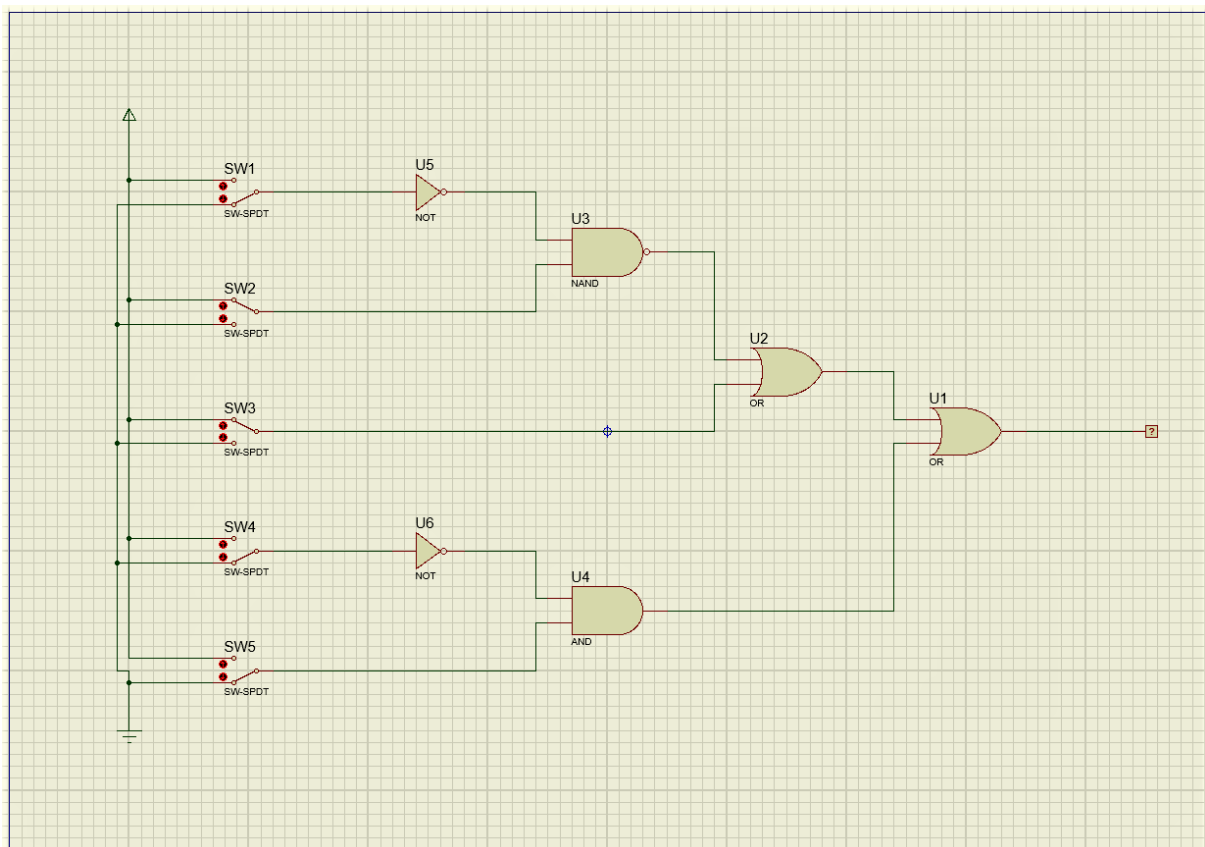

Picture 7.1. Set of gate for boolean function $F = (\neg(\neg A.B) + C) + (\neg D.E)$